



Practices for Chapter 7

A. Fill-in-blank:

1. "An asynchronous sequential logic circuit might not have a flip-flop". This statement is _____ (true/false).
2. "The basic RS flip-flop cannot be applied to implement asynchronous sequential logic circuits". This statement is _____ (true/false).
3. According to the circuit structure and the form of the input signal, the asynchronous sequential logic circuit has two types: _____ and _____.

B. Short Answer:

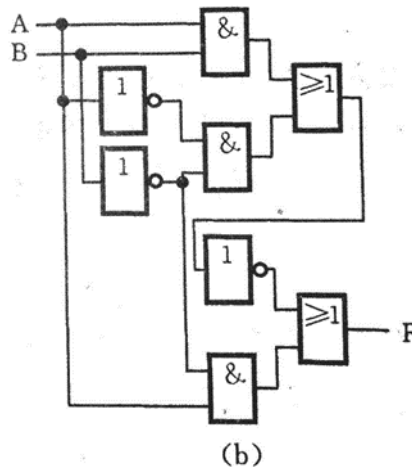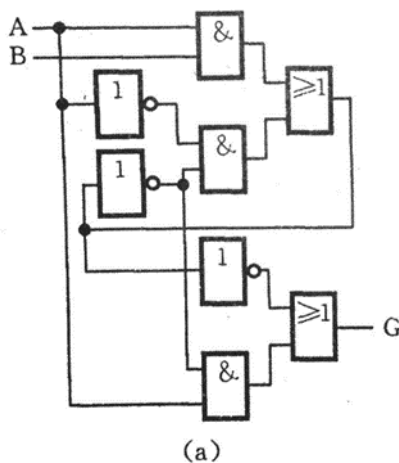1. Determine the 1)circuit types(Combine or Sequential) and 2) Mealy/Moore type of the following two figures:



C. Analysis

Please give the both next state table and diagram of the following figure:

