



Practices for Chapters 6 and 7

A. Fill-in-blank:

1. "An asynchronous sequential logic circuit might not have a flip-flop". This statement is _____ (true/false).
2. "The basic RS flip-flop cannot be applied to implement asynchronous sequential logic circuits". This statement is _____ (true/false).
3. According to the circuit structure and the form of the input signal, the asynchronous sequential logic circuit has two types: _____ and _____.
4. Typical devices of SSI include _____. Typical devices of MSI includes _____.
5. If a MSI device can convert decimal numbers (from 0 to 9) to its 4-bit BCD code, the name of such device is _____.
6. MSI denotes _____; VSI denotes _____; PLD denotes _____; CPLD denotes _____; VHDL denotes _____; and FPGA denotes _____.
7. A MSI device's pin arrangement diagram does not include the Vcc and GND information. This statement is _____ (true/false).

B. Short Answer:

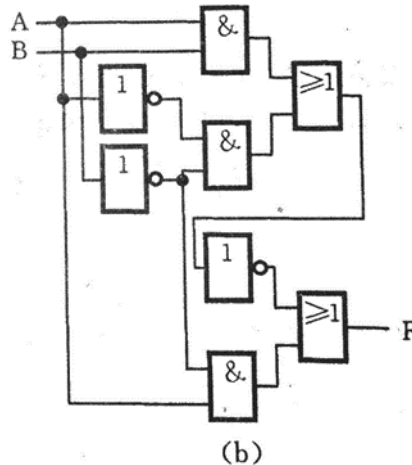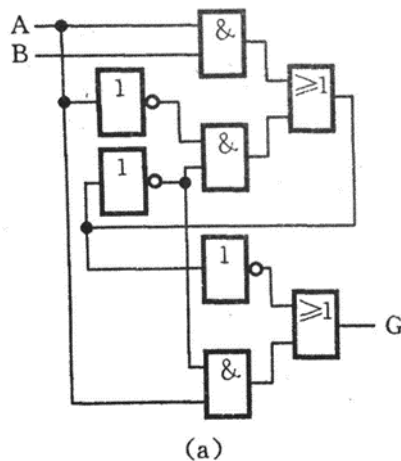1. Determine the circuit types of the following two figures:



2. Determine the function of the circuit:

